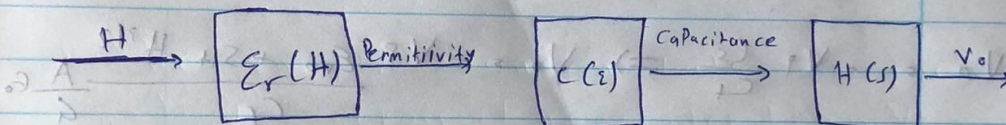


* Capacitive Measurement System homework

* Fahy Fraukh 217 11266

a) Draw a block diagram of the capacitive measurement system showing how the physical values flows in the system and the relationships between them

* Solution:-



b) Determine the relationship between the sensor capacity C_s and the relative humidity H

* Solution:-

$$C_s = \epsilon_r \epsilon_0 \frac{A}{d} = (\epsilon_{r0} + S_H \cdot H^{3/2}) \epsilon_0 \frac{A}{d}$$

c) ~~Determine the relationship between the sensor capacity~~

c) Determine the relationship b/w the output voltage V_o and the relative humidity

* Solution:

$$V_o \approx -V_p \frac{\frac{-1}{j\omega C_f}}{\frac{-1}{j\omega C_s}} = -V_p \frac{j\omega C_s}{j\omega C_f}$$

$$\Rightarrow V_o \approx -V_p \frac{C_s}{C_f} \Rightarrow V_o \approx -V_p \frac{E_{vo} + S_H H^{1/2}}{C_f} - \frac{A}{G} E_o$$